


ATTENUATION OF A RESISTIVE BRIDGE vs A HYBRID TRANSFORMER

Henry Hinrichs

PULSE INC.
Network Products Group

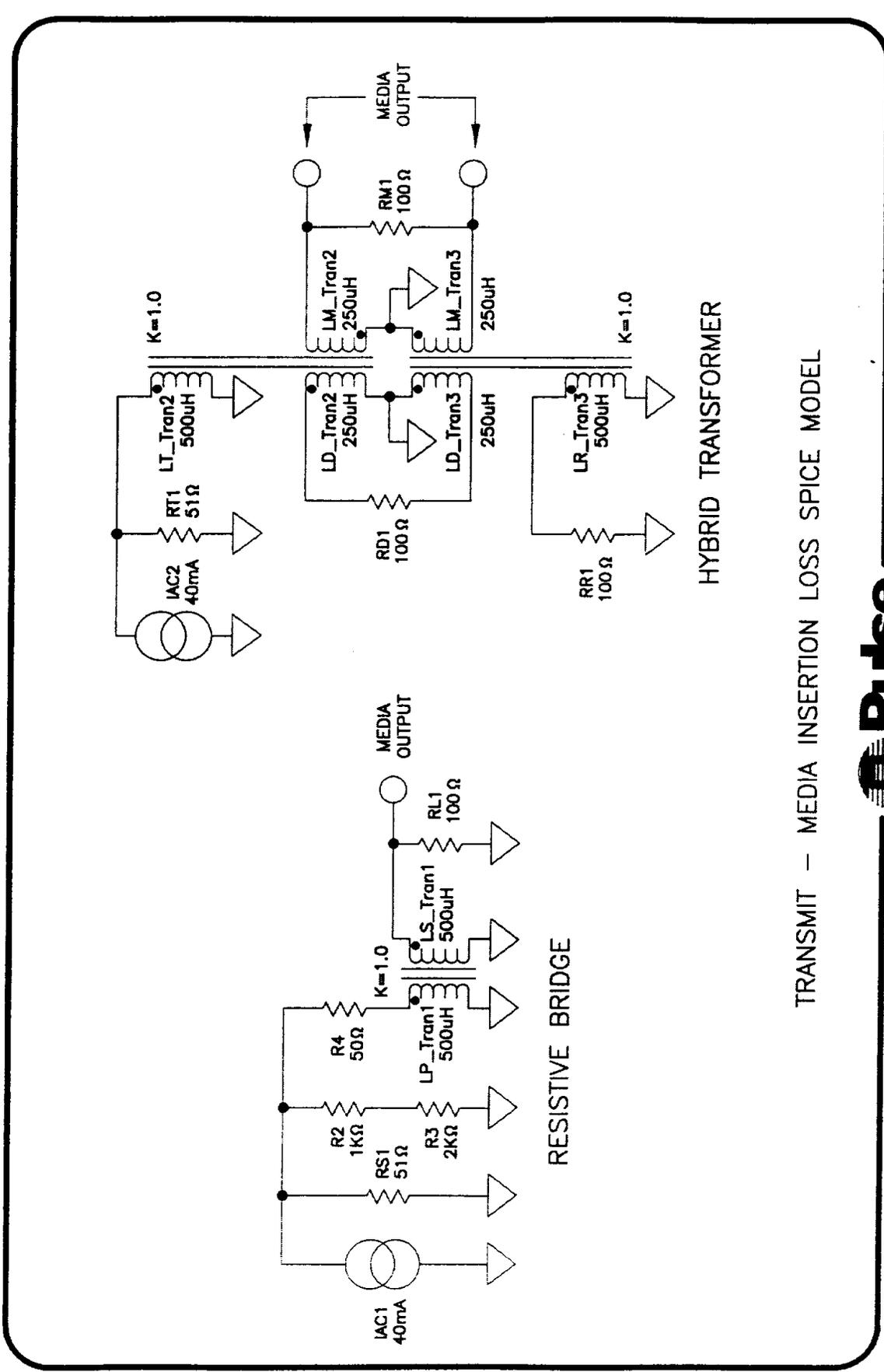12220 World Trade Dr.
San Diego, CA 92128
Phone: (619) 674-8100
FAX: (619) 674-8262






RESISTIVE BRIDGE


HYBRID TRANSFORMER

TRANSMIT – MEDIA INSERTION LOSS SPICE MODEL




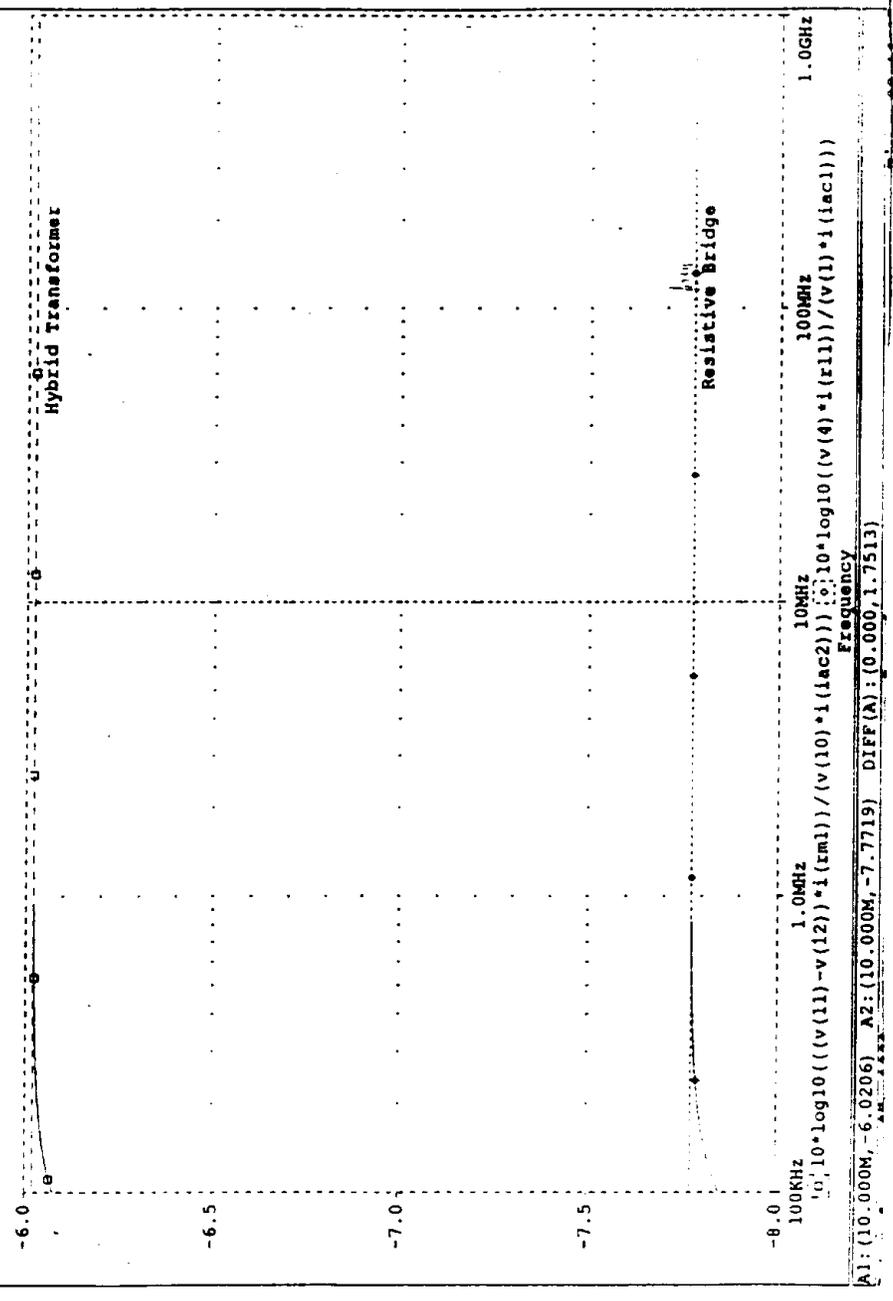Date/Time run: 01/07/98 08:55:21
 Transmit - Media attenuation, Bridge vs Hybrid Transformer
 Temperature: 27.0
 (A) C:\MSIM\BRIDGET.DAT



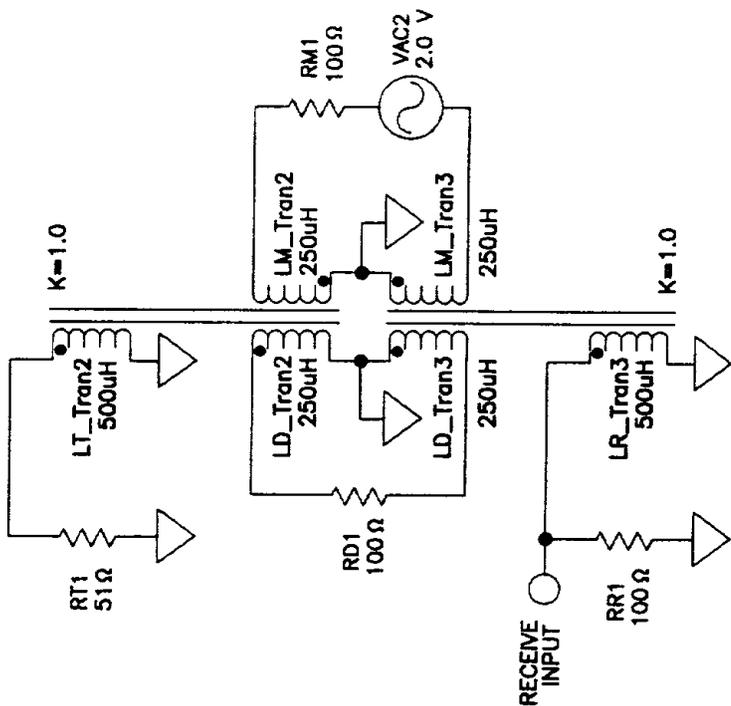

RESISTIVE BRIDGE

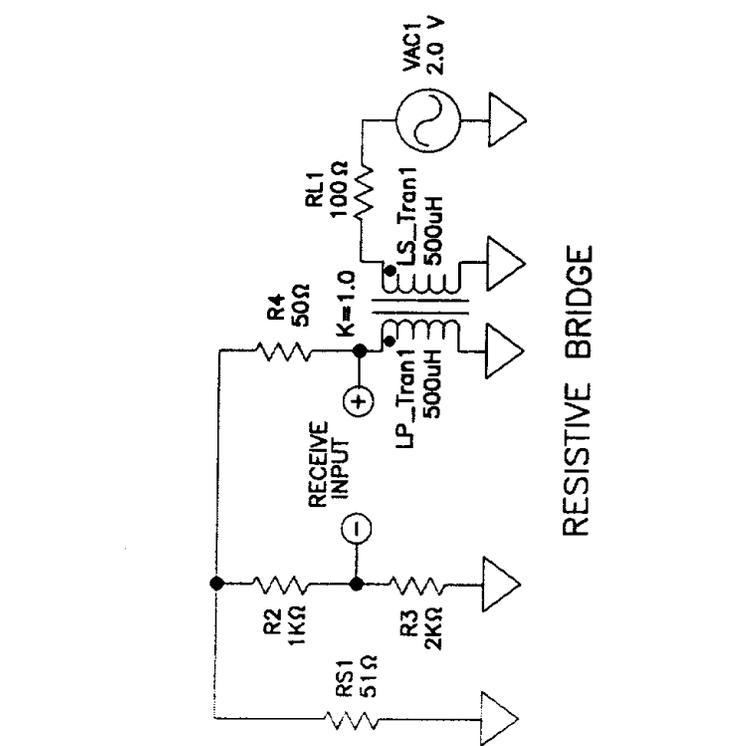


HYBRID TRANSFORMER

MEDIA - RECEIVE ATTENUATION SPICE MODEL



Date/Time run: 01/07/98 09:02:04
Media - Receive attenuation, Bridge vs Hybrid Transformer
Temperature: 27.0

(A) C:\MSIM\BRIDGER.DAT

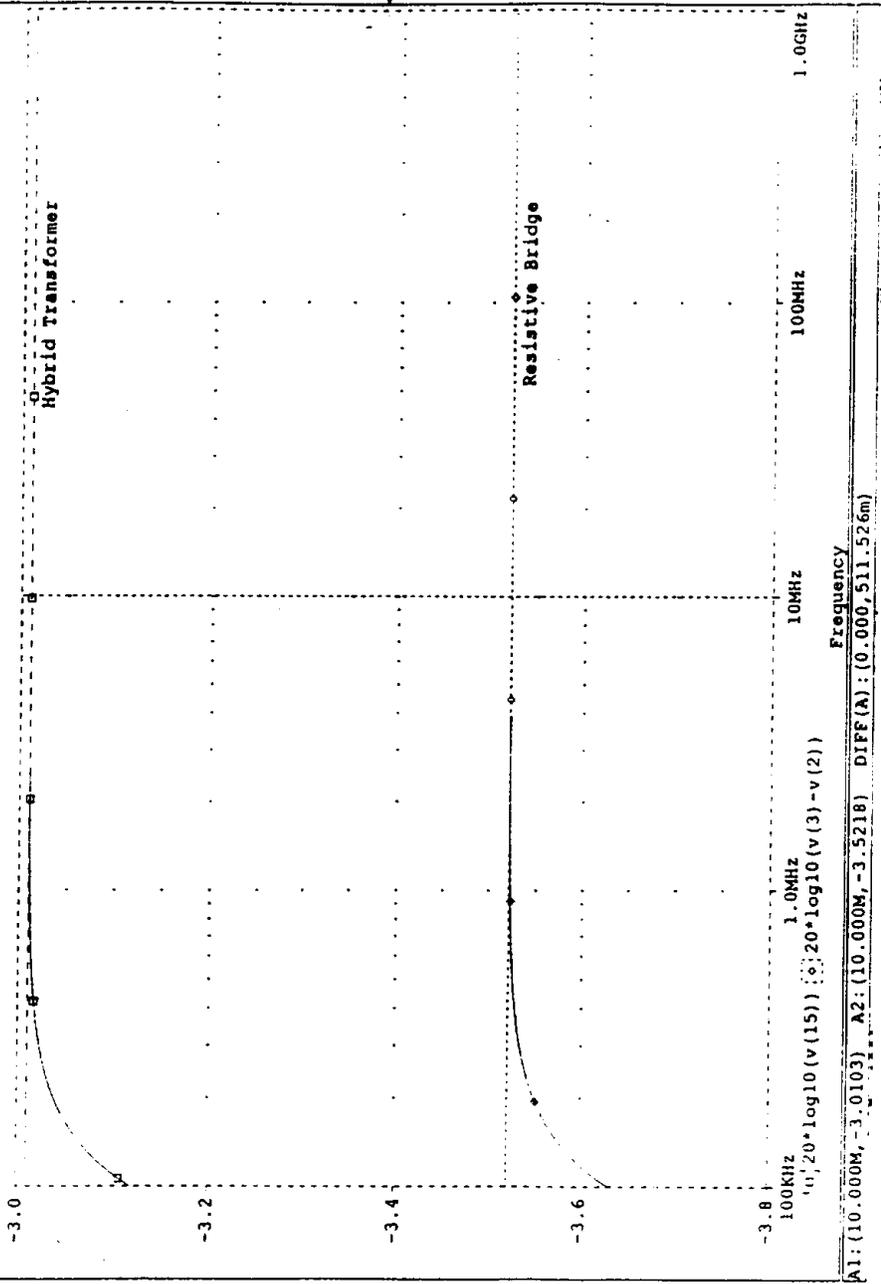

A1: (10.000M, -3.0103) A2: (10.000M, -3.5218) DIFF(A): (0.000, 511.526m)



Transmit - Media Insertion Loss (S21), Bridge vs Hybrid Transformer

* Synopsis: The following represents a side by side comparison of
* the transmit - media attenuation of a resistive bridge
* verses a hybrid transformer.

* Date: 01/07/98 H. Hinrichs
* Pulse Inc.
* 12220 World Trade Dr.
* San Diego, CA, 92128
* Tel (619) 674-8208
* FAX (619) 674-8262

* First the resistive bridge

```
IAC1 1 0 AC .02985 ; Stimulus, bridge
RS1 1 0 51
R2 1 2 1000 ; receive negative input
R3 2 0 2000
R4 1 3 50 ; receive positive input
* Transformer, 1:1 ratio with no high frequency parasitic losses
.param kval={1.0}
LP_Tran1 3 0 500uH
LS_Tran1 4 0 500uH
K_Tran1 LP_Tran1 LS_Tran1 {kval}
* Media port
RL1 4 0 100 ; Characteristic impedance of cable
```

* And now the Hybrid Transformer

```
IAC2 10 0 AC .02828 ; Stimulus, hybrid transformer
RT1 10 0 100
* Ideal hybrid transformer (again no parasitics)
* Note: Coil inductances establish the following port
* impedances:
* Transmit = 100 ohms
* Receive = 100 ohms
* Media = 100 ohms
LT_Tran2 10 0 500uH
LM_Tran2 11 0 250uH
LD_Tran2 13 0 250uH
K_Tran2 LT_Tran2 LM_Tran2 LD_Tran2 {kval}
LR_Tran3 15 0 500uH
LM_Tran3 12 0 250uH
LD_Tran3 0 14 250uH
K_Tran3 LR_Tran3 LM_Tran3 LD_Tran3 {kval}
RR1 15 0 100 ; Receive port terminated in 100 ohms
RD1 13 14 100 ; Dummy 100 ohm resistive load
RM1 11 12 100 ; Media port terminated in 100 ohms
```

```
.probe
.ac dec 100 100k 200meg
.end
```

Media - Receive attenuation, Bridge vs Hybrid Transformer

* Synopsis: The following represents a side by side comparison of
* the media - receive attenuation of a resistive bridge
* verses a hybrid transformer.

* Date: 01/07/98 H. Hinrichs
* Pulse Inc.
* 12220 World Trade Dr.
* San Diego, CA, 92128
* Tel (619) 674-8208
* FAX (619) 674-8262

* First the resistive bridge

```
RS1  1    0    51
R2   1    2   1000 ; receive negative input
R3   2    0   2000
R4   1    3    50  ; receive positive input
* Transformer, 1:1 ratio with no high frequency parasitic losses
.param kval={1.0}
LP_Tran1  3    0    500uH
LS_Tran1  4    0    500uH
K_Tran1   LP_Tran1  LS_Tran1  {kval}
* Media port
RL1  4    5    100  ; Characteristic impedance of cable
* Note: 1/2 of stimulus is dropped across far end source
VAC1 5    0    AC    2
```

* And now the Hybrid Transformer

```
RT1  10    0    100
* Ideal hybrid transformer (again no parasitics)
* Note: Coil inductances establish the following port
* impedances:

* Transmit = 100 ohms
* Receive = 100 ohms
* Media = 100 ohms
LT_Tran2  10    0    500uH
LM_Tran2  11    0    250uH
LD_Tran2  13    0    250uH
K_Tran2   LT_Tran2  LM_Tran2  LD_Tran2  {kval}
LR_Tran3  15    0    500uH
LM_Tran3  12    0    250uH
LD_Tran3  0     14   250uH
K_Tran3   LR_Tran3  LM_Tran3  LD_Tran3  {kval}
RR1  15    0    100 ; Receive port terminated in 100 ohms
RD1  13    14   100 ; Dummy 100 ohm resistive load
RM1  11    16   100 ; Media port terminated in 100 ohms
* Note: As with the bridge circuit 1/2 of stimulus is dropped across
* far end source
VAC2 16    12   AC    2

.probe
.ac dec 100 100k 200meg
.end
```