




Error Propagation with DFE's.

Mike Dudek QLogic


IEEE 802.3by Presented to ad-hoc 12/16/15

- **Error Propagation with the use of DFE's is a known issue that can create error bursts. This presentation explores the error propagation mechanism and suggests what criterion should be used to reduce this effect.**
- **For ease of explanation it is assumed in the following that the initial error is a "zero" erroring to a "one". The analysis is the same for a "one" erroring to a "zero" but trying to consider both at the same time makes explanation more difficult.**
- **For the initial analysis it is assumed that the first tap is negative sign which is the typical situation. In COM the "b" values are the opposite sign to the classic tap weight so this is the positive b1 condition.**

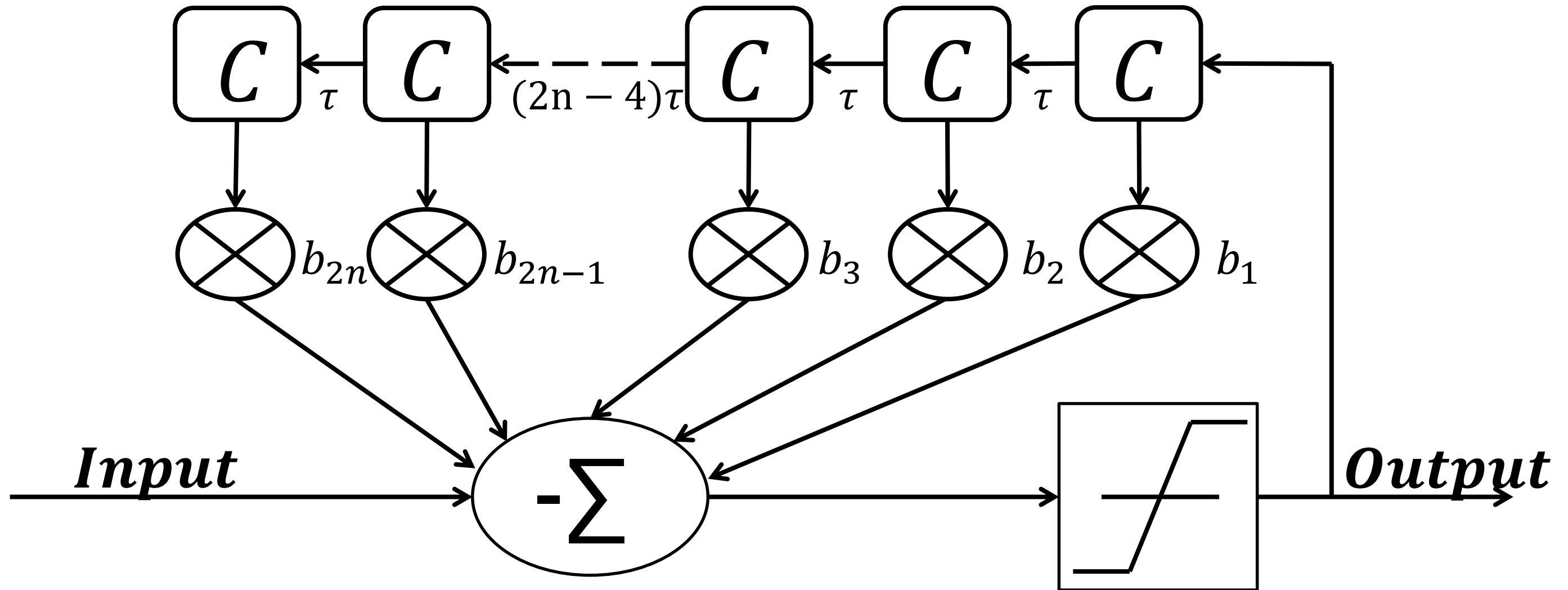


- The summing junction is labelled as negative because that is how COM analyzes it.
- C indicates a correct bit.
- The DFE taps are assumed to be set such that they remove the ISI caused by the applicable previous bit.

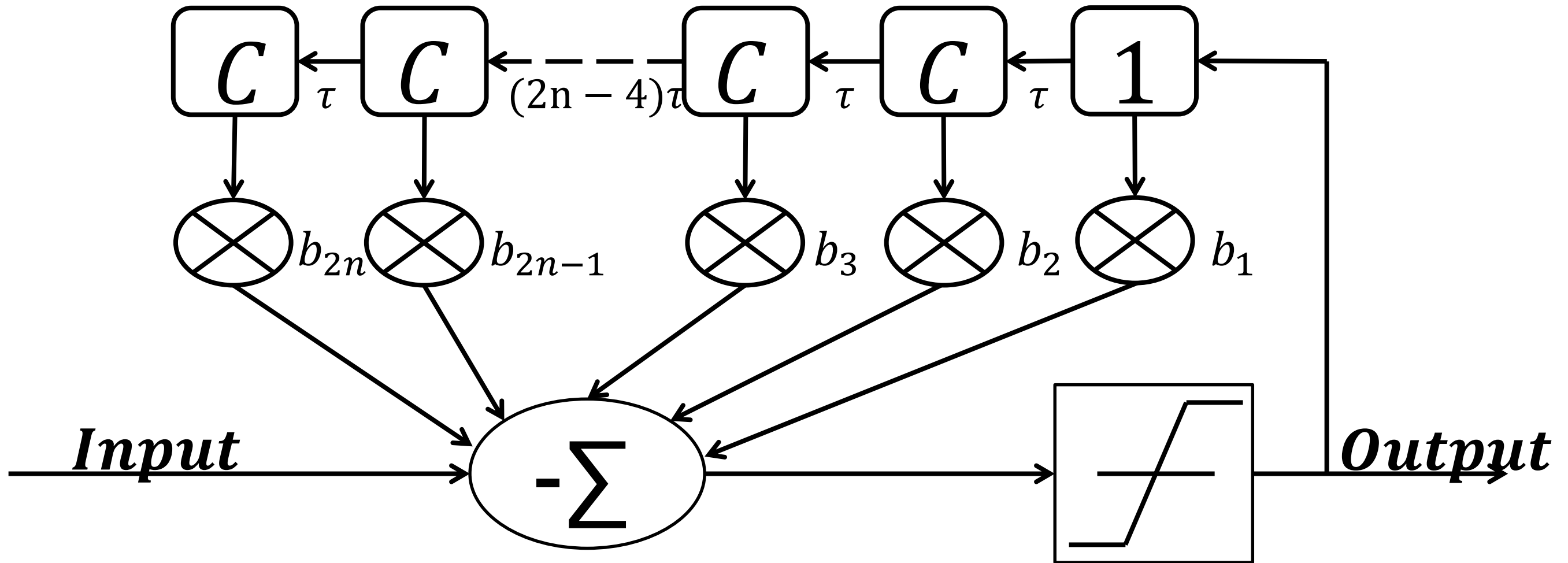When the initial bit has errored from a “zero” to “one”




- With b_1 positive if the next input bit is a zero the input to the slicer will be even more negative and the probability of an error becomes very low
- If the next input bit is a one then the signal into the slicer becomes smaller and the probability of it being detected as a “zero” becomes larger.
 - If b_1 is 1 the input signal is at the normal “zero” level and the probability of it being detected as zero is almost 100%.
 - If b_1 is 0.5 the input signal to the slicer will be at the slicer level and the probability of error is 50%.

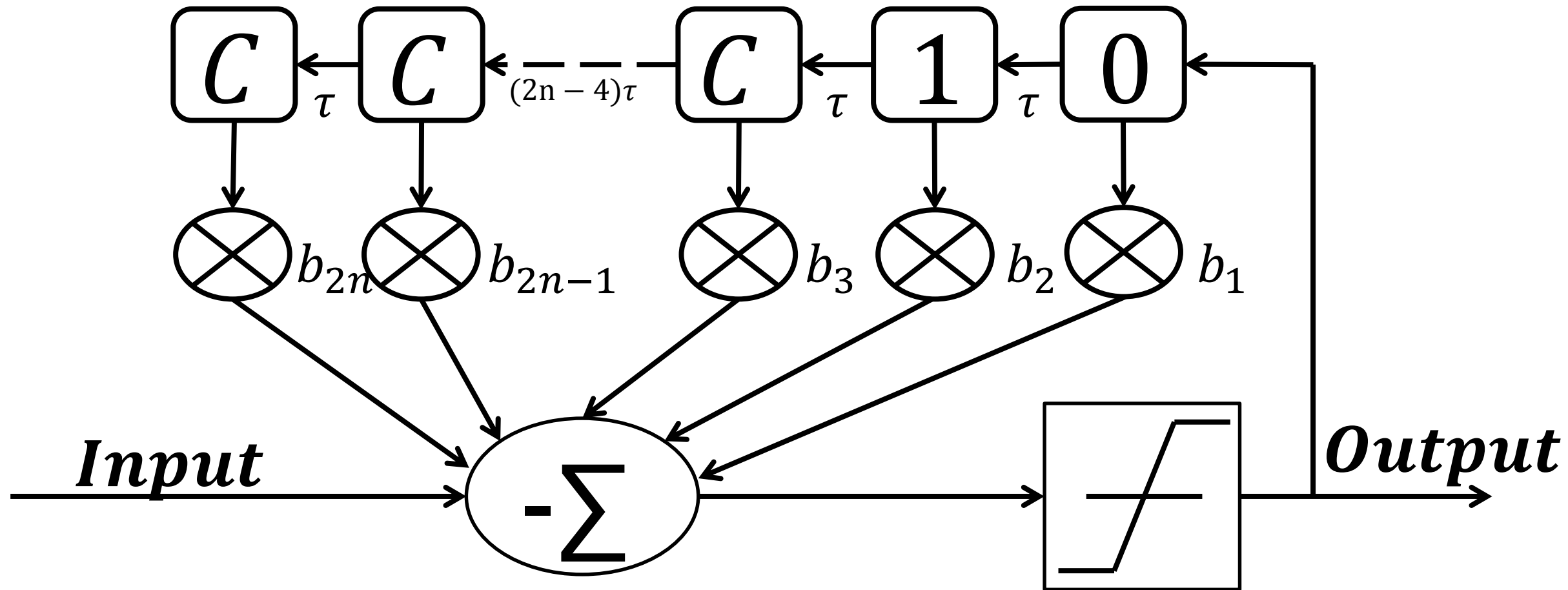When the error has propagated to the second bit.




- With b_1 positive the feedback from the first tap to the slicer will be positive and the feedback from the second tap will depend on b_2 . If b_2 is also positive then the feedback error will be smaller. If b_2 is negative the feedback error will be larger.
 - The feedback error is $b_2 - b_1$ and is likely to be negative. (It will be if b_1 is positive and dominant.)
- If the next bit is a zero and $b_2 - b_1$ is negative then the signal into the slicer becomes larger and the probability of error becomes larger.
 - If $(b_1 - b_2)$ is 1 then the probability of error is close to 100%.
 - If $(b_1 - b_2)$ is 0.5 the input signal to the slicer will be at the slicer level and the probability of error is 50%.
- If the next bit is a one and $b_1 - b_2$ is positive the probability of error is very low.

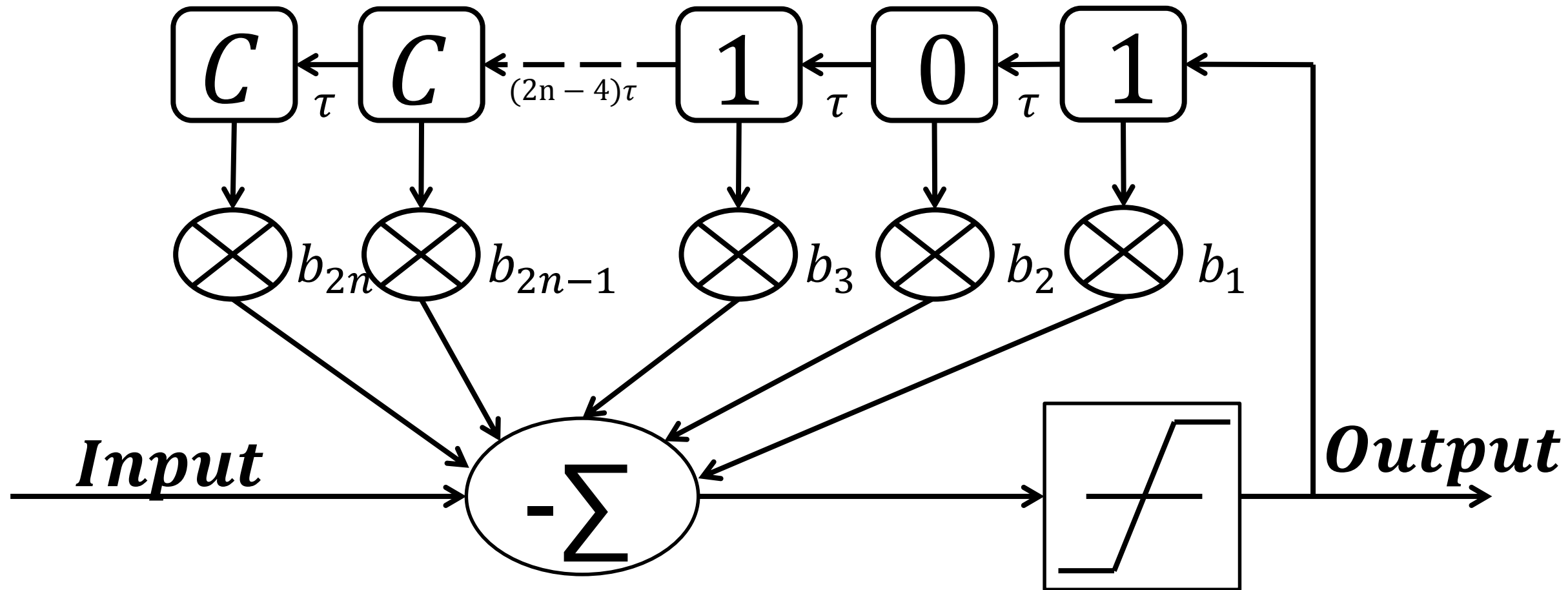When the error has propagated to the third bit.



- The error in the feedback is now equal to $b_1 - b_2 + b_3$.
- If the next bit is a one and $b_1 - b_2 + b_3$ is positive then the signal into the slicer becomes smaller and the probability of error becomes larger.
 - If $(b_1 - b_2 + b_3)$ is 1 then the probability of error is close to 100%.
 - If $(b_1 - b_2 + b_3)$ is 0.5 the input signal to the slicer will be at the slicer level and the probability of error is 50%.
- If the next bit is a zero and $b_1 - b_2 + b_3$ is positive then the signal is even more negative and the probability of error is very low.

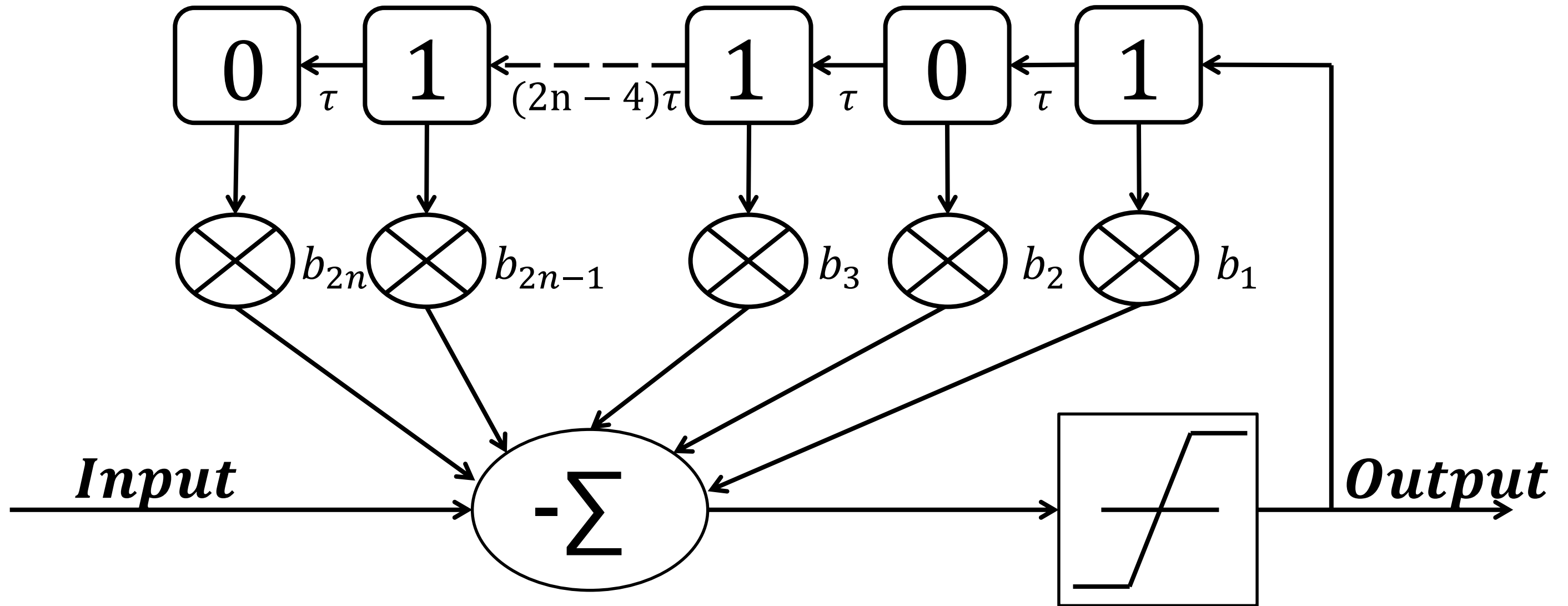When errored bits have filled the shift register.



Analysis when errors have filled the shift register


- The feedback amount at the slicer is

$$\sum_{m=1}^n b_{(2m)} - \sum_{m=1}^n b_{(2m-1)}$$

- In order to create problems the bursts generally need to be long such that the shift register is full of this errored bit pattern. We should therefore ensure that the errors don't propagate at a very high probability in this condition.
- The existing criterion of having $\text{Mod } bn$ for all the taps of <0.35 or <0.5 does not do this. (with $b_1=0.35$, and $b_2=-0.35$ even if all the other taps are zero there is a very high probability of very long error bursts.
- The proposed criterion to limit error propagation is

$$\sum_{m=1}^n b_{(2m)} - \sum_{m=1}^n b_{(2m-1)} < 0.5 \text{ or } \sum_{m=1}^{2n} b_m * (-1)^{(m-1)} < 0.5$$

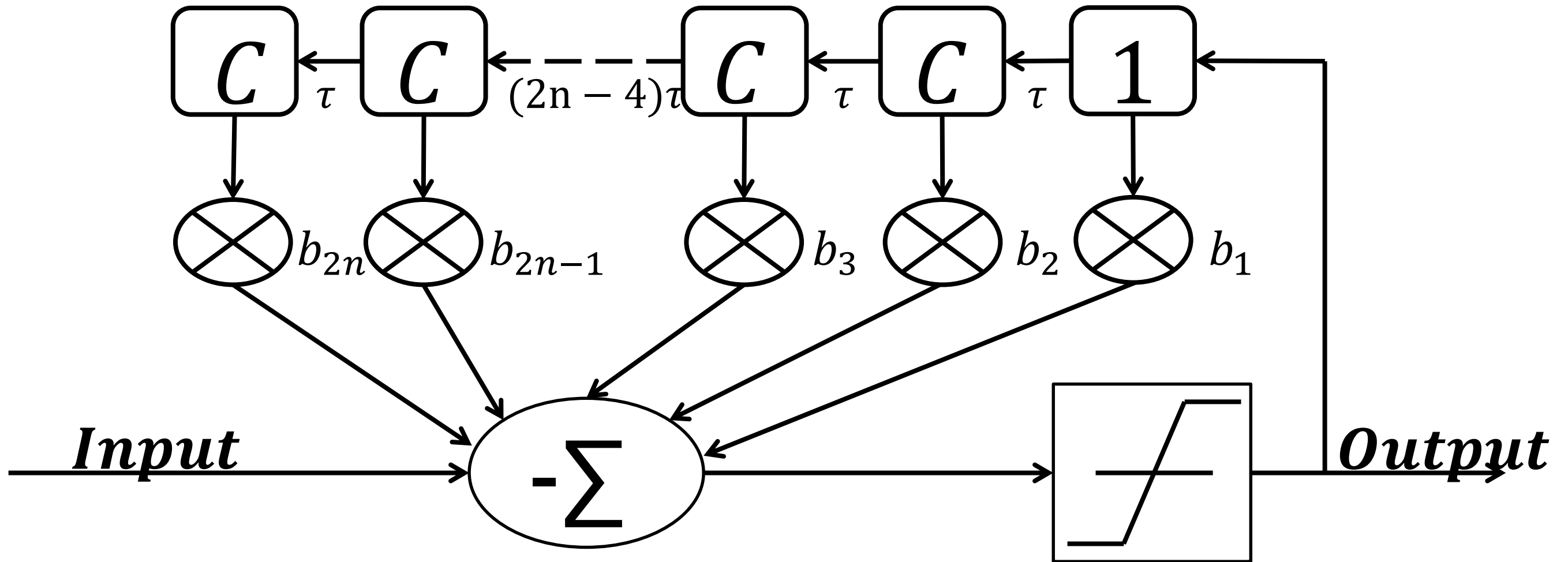Other considerations. If b1 is negative, and initial error is “Zero” mistaken as “one”



- With b1 negative if the next input bit is a one the input to the slicer will be even more positive and the probability of an error becomes very low
- If the next input bit is a Zero then the signal into the slicer becomes larger and the probability of it being detected as another “one” becomes larger.
 - If b1 is 1 the input signal is at the normal “one” level and the probability of it being detected as one is almost 100%.
 - If b1 is 0.5 the input signal to the slicer will be at the slicer level and the probability of error is 50%.

Analysis when errors have filled the shift register with b1 positive.

- For the error propagation to occur the shift register will get filled with all “ones” (or all “zeros” if the original error had been a “one” mistaken as a “zero”)
- The feedback amount will be


$$\sum_{m=1}^{2n} b_{(m)}$$

- The criterion to limit error propagation would be

$$\sum_{m=1}^{2n} b_{(m)} > -0.5$$

- This is however a very unlikely scenario and I doubt if it is worth complicating the specification by adding it.

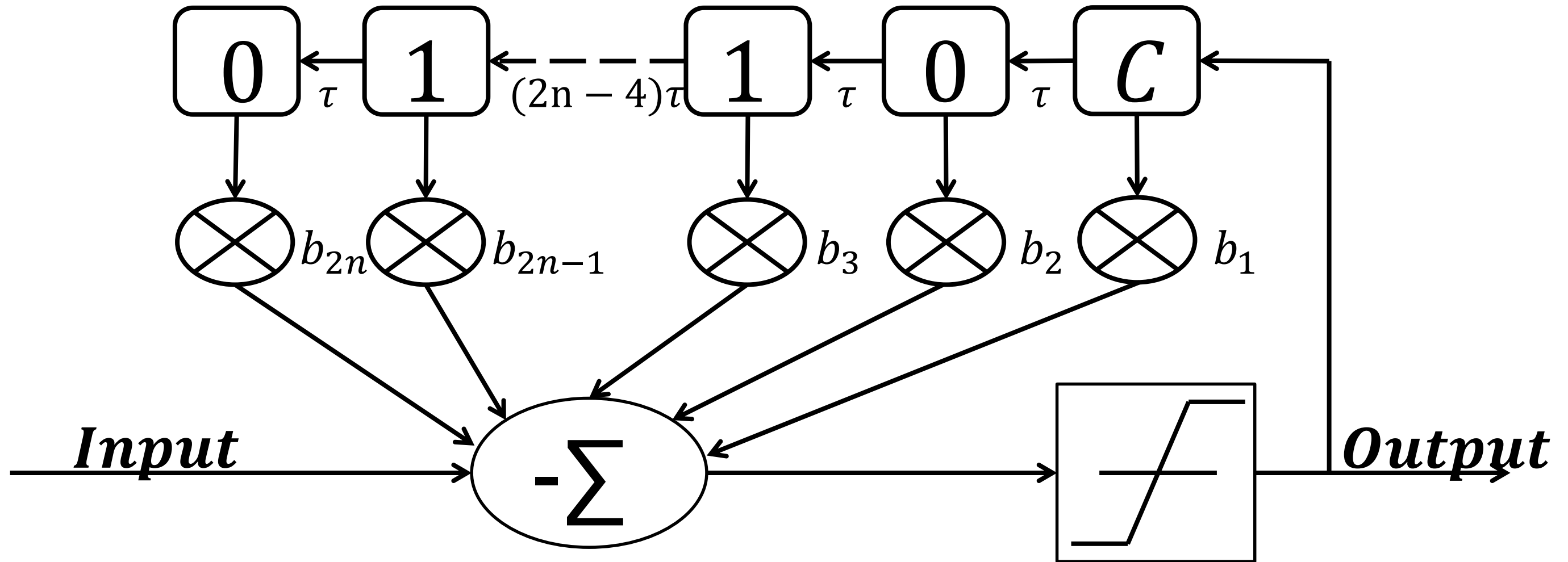Other considerations. If the input sequence is 0101010111010



- When the second adjacent one is input the correct decision will be made and the shift register will look as above.

Analysis of 0101010111010

- The feedback error is now

$$\sum_{m=1}^n b_{(2m)} - \sum_{m=1}^{n-1} b_{(2m+1)}$$

- If this is 0.5 the probability of error is still 50%. The error burst will restart. It will just have one correct bit in the middle of a block of errors.