


PoDL Considerations for MDI Return Loss Mask

Andrew Gardner

- ▶ Review basic PoDL MDI/PI architecture
- ▶ Discuss limitations on PoDL inductors
- ▶ Review some data from bhagwat_3ch_02a_0718.pdf
- ▶ Propose next steps


- ▶ Low frequency return loss a function of :
 - DC blocking capacitors C1/C2
 - PoDL inductors L1/L2
- ▶ Low frequency return loss dominated by L1/L2 when the MDI/PI is over-damped:

$$C \gg \frac{L}{(50\Omega)^2}$$

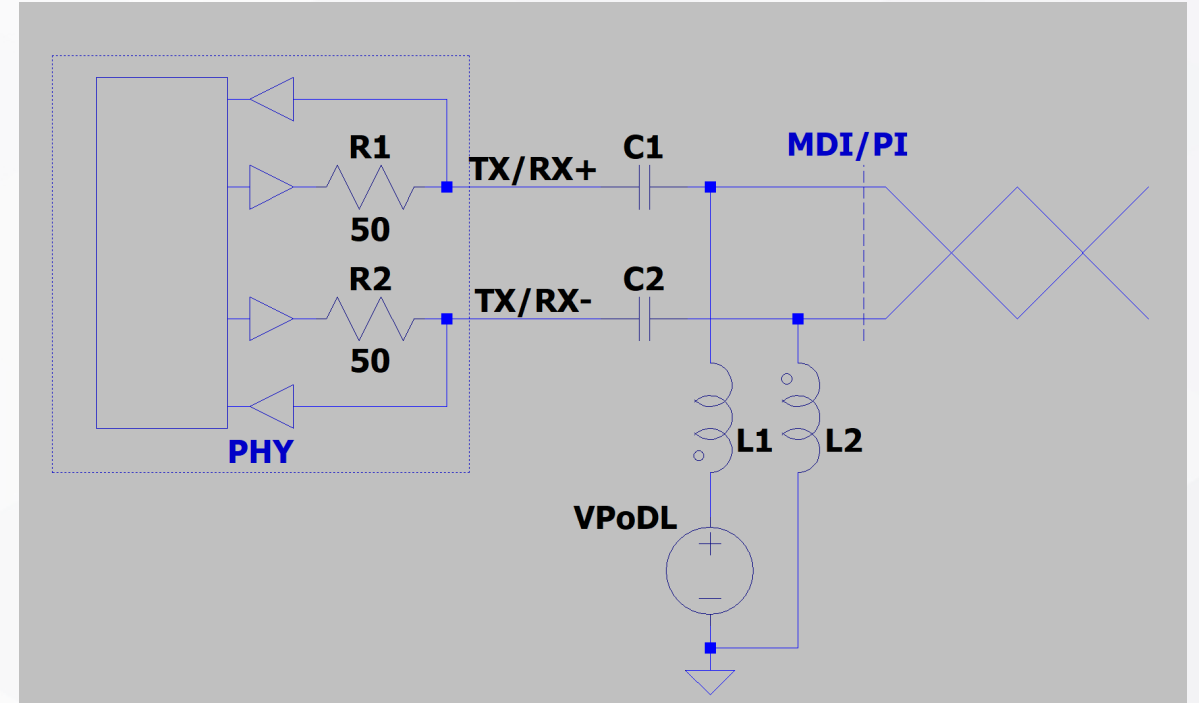

- ▶ PoDL inductor selection is a balancing act
 - Size and cost goes as
 - Open-circuit inductance (OCL)
 - Square of ampacity, e.g. doubling ampacity quadruples size and cost
 - Low-frequency RL mask constrains OCL
 - OCL also constrained by droop
 - High-frequency RL mask constrains inductor self-resonant frequency (SRF)
 - Mid-band RL constrains inductor core-loss and use of snubber resistors and/or common-mode terminations

Typical MDI Return Loss Mask


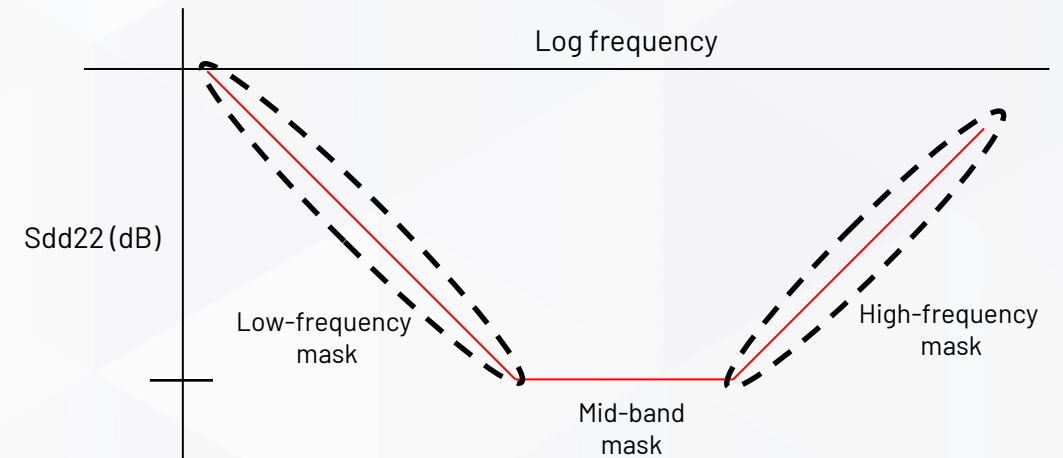


Note: Sdd22 and RL are used interchangeably here even though RL is a positive quantity while Sdd22 is negative



- ▶ Parasitic capacitance between inductor terminals limits high frequency impedance
- ▶ Maximum inductor impedance occurs at:

$$SRF = \frac{1}{2 * \pi * \sqrt{L * C_{parasitic}}}$$

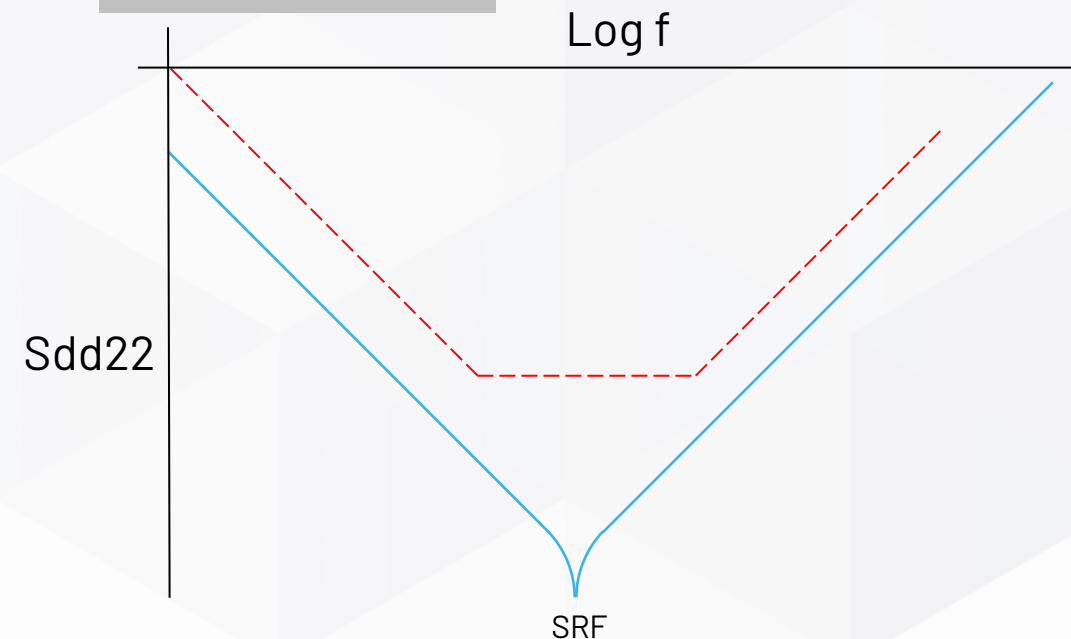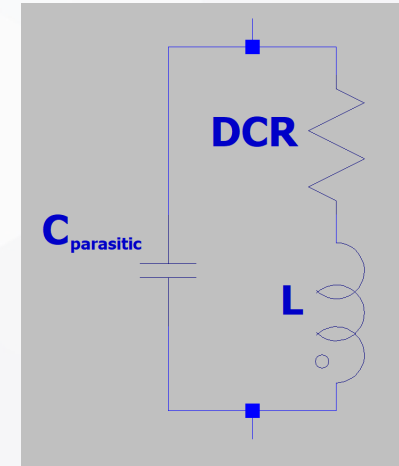- ▶ SRF manifests itself as a 'V' in the observed RL
- ▶ Bigger inductors and inductors with higher OCL have lower SRF
- ▶ Core-loss can also cause inductor impedance to drop off at high frequencies





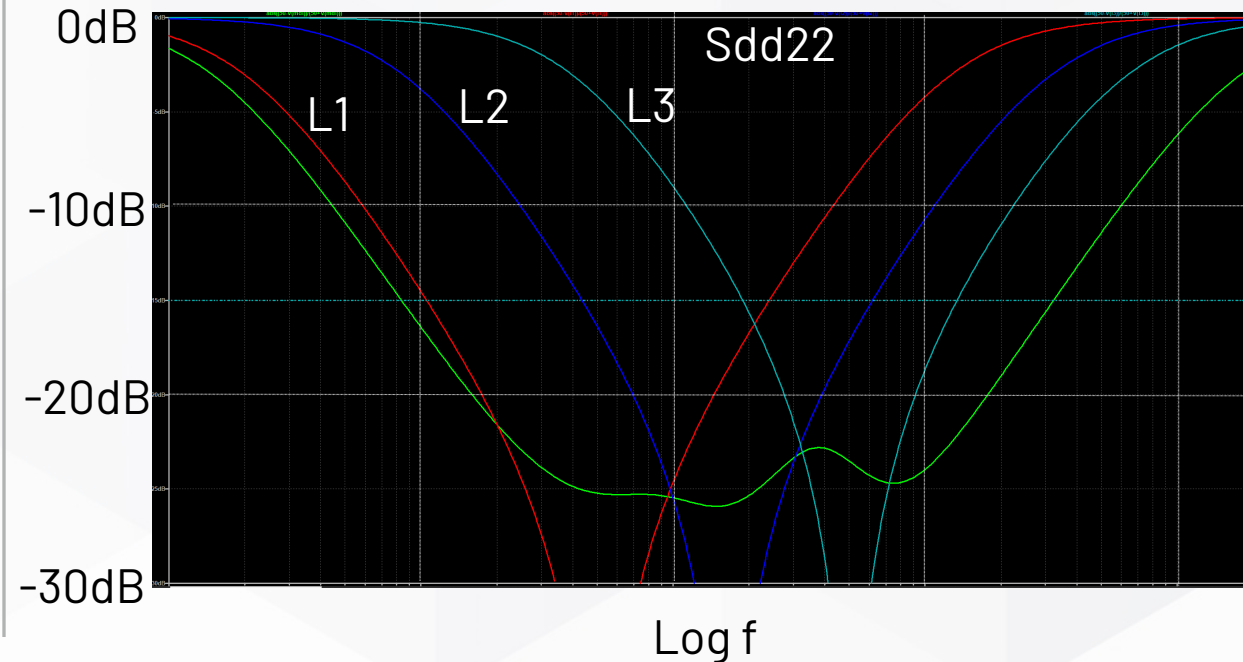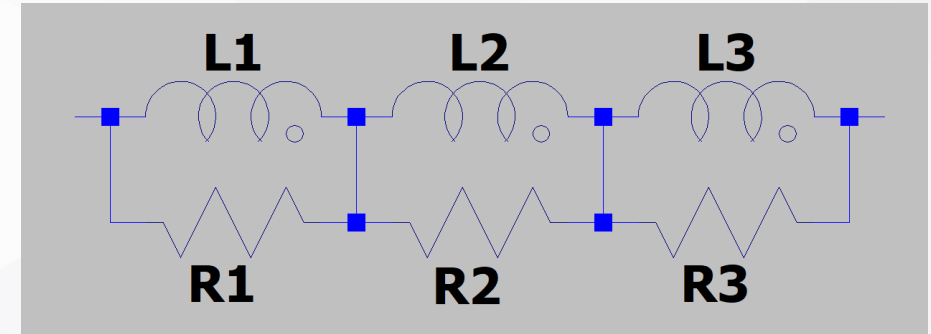- ▶ What happens if SRF fails to meet high frequency RL mask?
 - Inductor cascades can be employed to extend return loss
 - Cascade inductors are smaller relative to first inductor, but cost and complexity increase can be significant
 - Meeting 20dB mid-band RL may be problematic depending on snubber resistor R1/R2/R3 requirements and core-loss



- ▶ PoDL inductors can be a source of mode conversion at the MDI
- ▶ Low frequency mode conversion is a function of L1/L2 OCL matching
 - Can be mitigated with PoDL power path CMC
 - Some newer inductors offer improved matching specs
- ▶ Larger footprint inductors tend to have poor high-frequency mode conversion loss
 - High-frequency mode conversion may be mitigated with cascades

RL Data for Off-the-Shelf Inductor

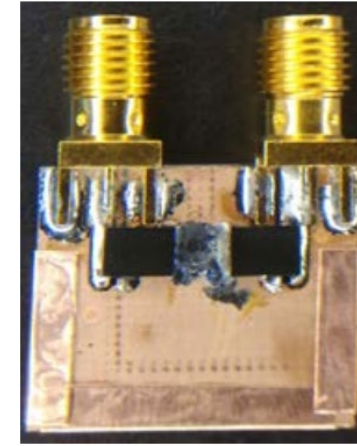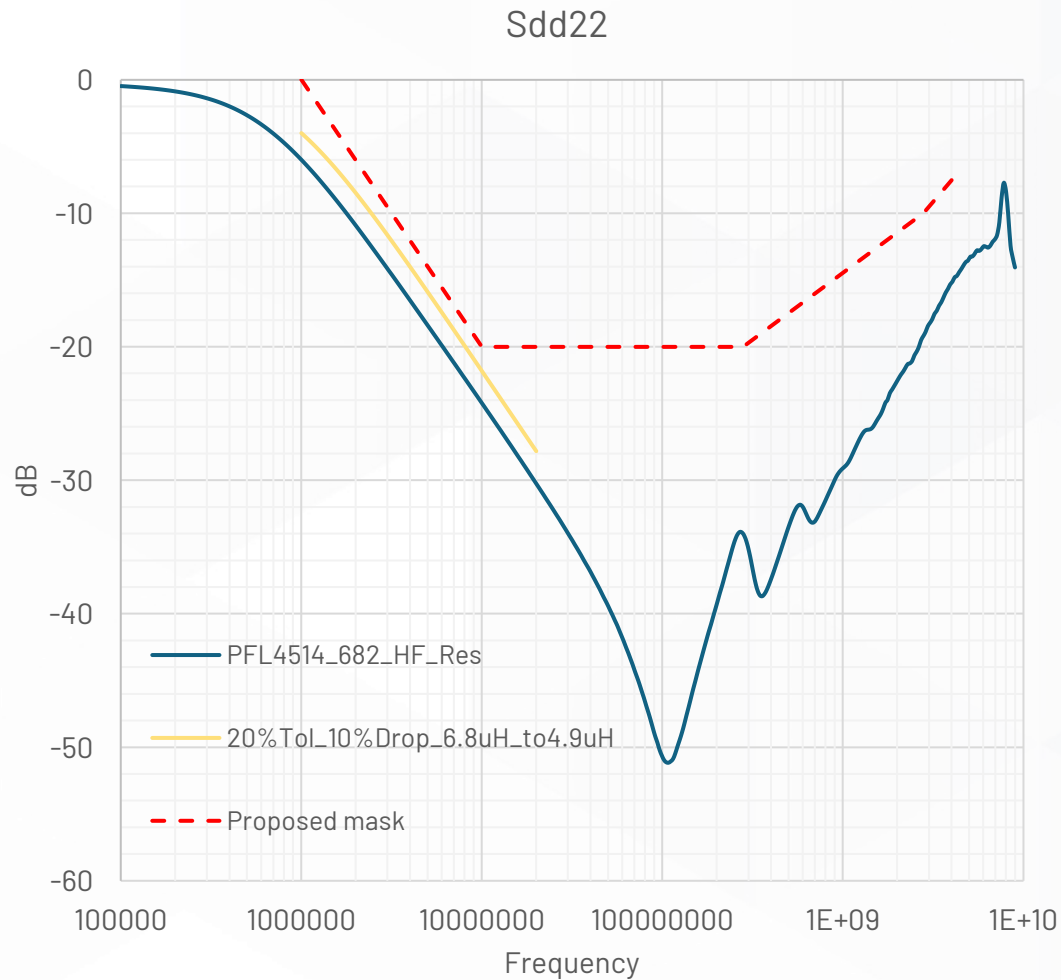

PFL4514-682

- ▶ Data originally presented in bhagwat_3ch_02a_0718.pdf
- ▶ RL data does not include effects of PHY and other MDI components
- ▶ 3.4mm x 4.9mm x 1.4mm footprint
- ▶ D/S ampacity: 0.86A DC at 105C ambient

- ▶ Identify inductor ampacity requirements
- ▶ Design and Build test fixtures
 - Measure RL and mode conversion with VNA
 - Evaluate ampacity
- ▶ Present results and propose MDI RL mask modifications as needed