



Current Limit Versus Energy Limit Based PSE

Thong Huynh
Maxim Integrated Products



Review of PoE+ System Consideration

- **PoE+ System Requirements:**
 - System Inter-Operability
 - Allow Safe Maximum Possible Power Delivered from PSE to PD
 - Adhere to the Maximum Current Allowed *:
 - In the Cable
 - In the Connector
 - In the Patch Panel
 - In the LAN Magnetics
 - Backward Compatible w/ 802.3af Legacy Devices
 - Support 180uF capacitor on PD
 - Simplify Compliant Testing

***Note: Maximum current value for cable, connector, and patch panel are determined by heating effect which causes by DC/RMS current. Low level transient current that lasted less than a few seconds does not cause significant heating and could be neglected**





Review of PoE+ System Consideration

- **PSE Requirements:**
 - PD Detection, L1 Classification, Optional L2 Classification
 - Handle Input Power Supply Voltage Transient
 - Protect Port Short Circuit Condition
 - Provide as Much Power as Possible to the PD, Limited only by the Cable Capability
- **PD Requirements:**
 - Provide Detection and Classification Signatures
 - Manage Input Ripple Current
 - Handle Load Step Transient
 - Utilize as Much Power as Possible from the PSE When the Application Requires






 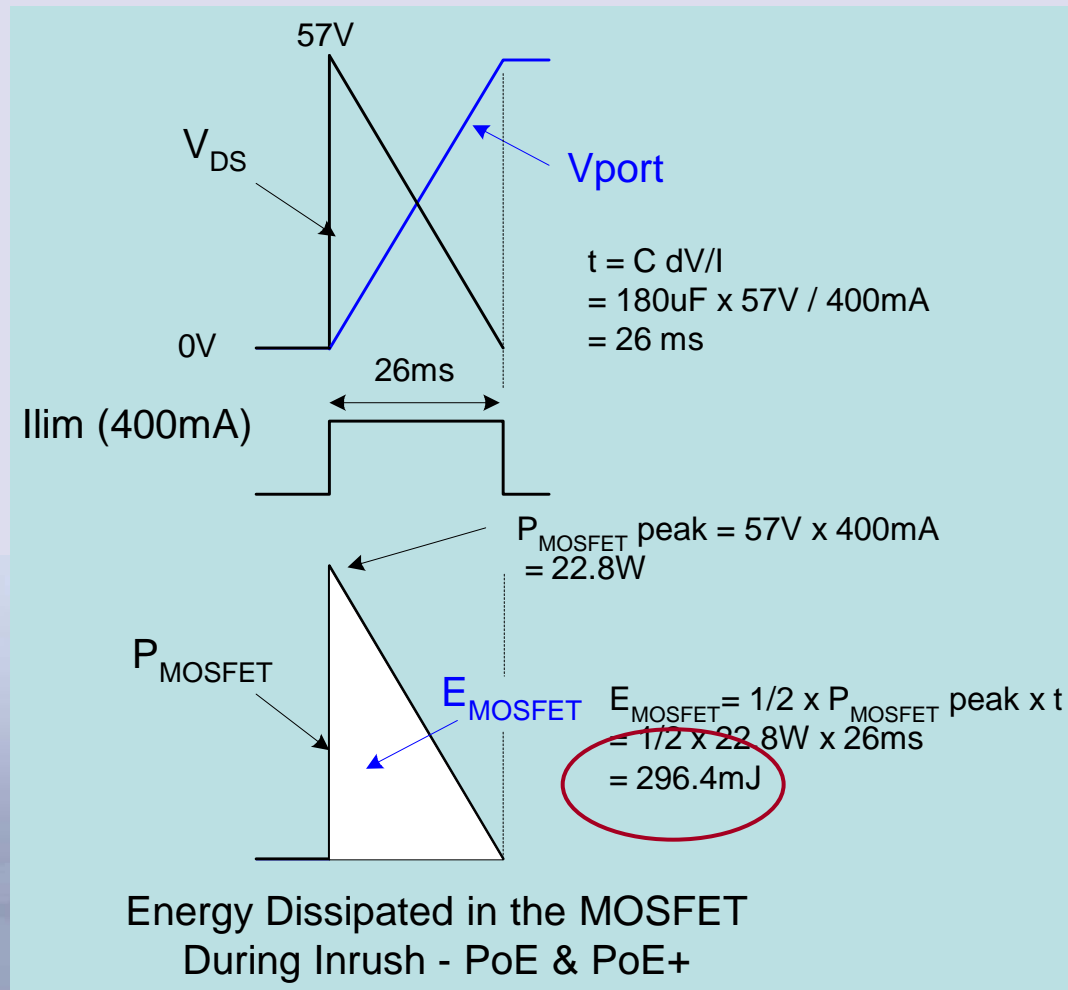MOSFET Power Dissipation – During Inrush Period for Both PoE and PoE PSEs






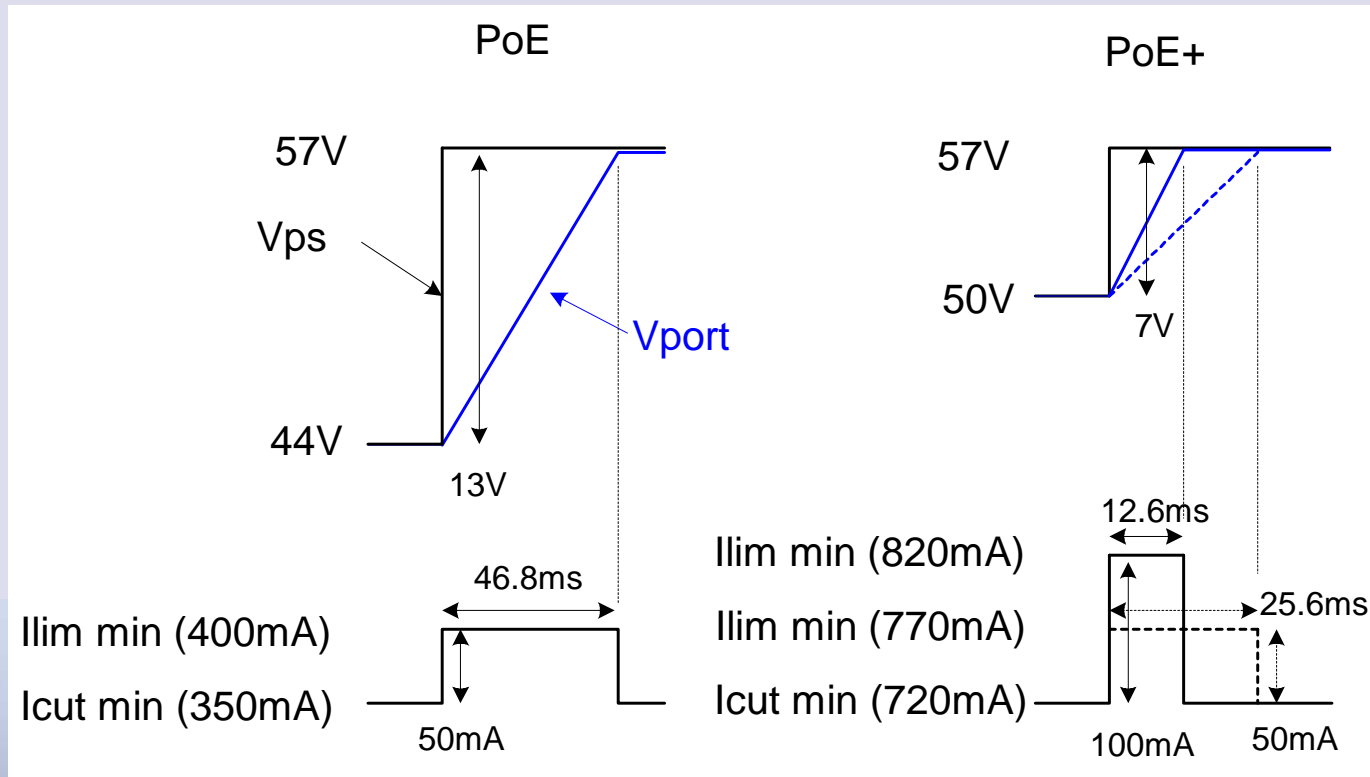Current Limit Based - Input Voltage Transient:




 In PoE+ system, there is plenty of head room to handle input transient and PD load step at the same time





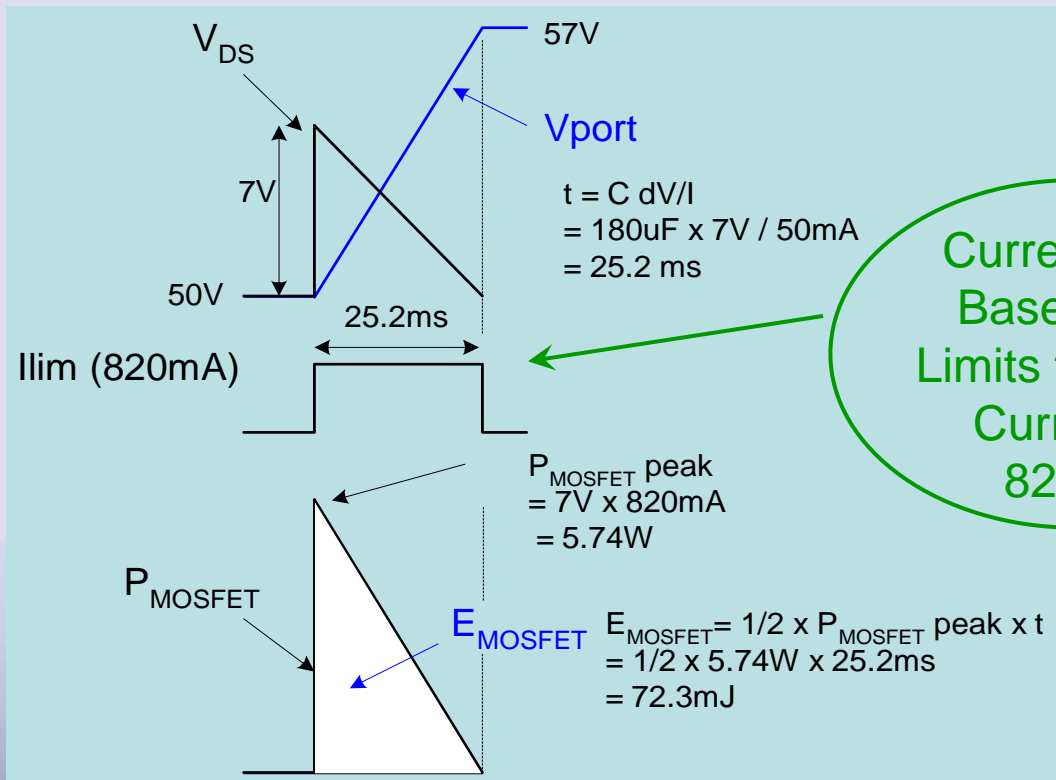Current Limit Based - MOSFET Power Dissipation – During Input Transient for PoE+ PSE



Current Limit Based PSE Limits the Peak Current to 820mA

Energy Dissipated in the MOSFET During Input Transient and PD Load Step, Allowing 50mA Load Step above PD maximum average current for 50ms - PoE+






Current Limit Based – Output Short Circuit

Current Limit Based PSE Limits the Peak Current to 820mA



MOSFET Power Dissipation Calculation

 

→ MOSFET Power Dissipation Dominates During Inrush Period



Truth or Myth?

Current Limit Based Causes Higher Power Dissipation in the Power MOSFET in PoE+ System? → **Myth**

- **The Truth is:**

- Power Dissipation in the MOSFET is Largest During the Inrush Period. This Power Dissipation is the **same** for **PoE** and **PoE+** Systems, Whether **Current Limit** or **Energy Limit** Based is used.
- This Large Power Dissipation During Inrush is What Has Been Impeding the Integration of the Power MOSFET in the PSE Controller.



Energy Limit Based - Input Voltage Transient

- **Short Cable:**

- $R_{\text{cable}} = 1.0\Omega$ (estimated: includes all PSE power path impedances)
- Input Voltage Transient from 50V to 57V
- dV/dt maximum = 3.5V/us
- PD capacitance = 180uF
- Peak Current Due to $dV/dt = 180\mu\text{F} \times 3.5\text{V}/\mu\text{s} = 630\text{A!} \rightarrow$
Peak Current is Limited Only by $R_{\text{cable}} = (57\text{V} - 50\text{V})/1.0\Omega =$
7A

Energy Limit
Based PSE
Does Not Limit
the Peak
Current!



Energy Limit Based - Output Short Circuit

- **Short Cable:**

- $R_{\text{cable}} = 1.0\Omega$ (estimated: includes all PSE power path impedances)
- Input Voltage = 57V Maximum


- \rightarrow Peak Current is Limited Only by $R_{\text{cable}} = 57\text{V}/1.0\Omega = 57\text{A}$

Energy Limit
Based PSE
Does Not Limit
the Peak
Current!



Energy Based PSE - Testability

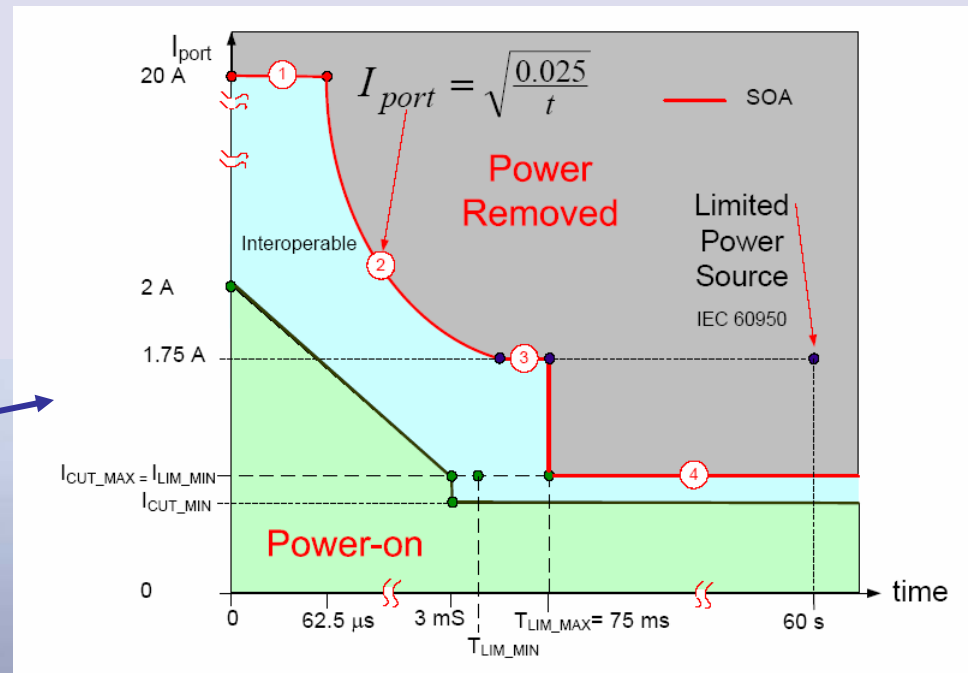- Energy Based PSE Dictates Complex Model for Testing



Graph is from the Vport Ad-Hoc presentation



Current Limit vs Energy Limit for PoE+ PSE

	Current Limit	Energy Limit	Advantages/Problem
MOSFET Power Dissipation During Inrush	246.4mJ	246.4mJ	Same
Peak Current During Input Transient short cable	820mA (920mA Maximum)	7A	Current is guaranteed to be limited High current peak can saturate and possibly damage the LAN Magnetics
Peak Current During Output Short Circuit	820mA (920mA Maximum)	57A	Current is guaranteed to be limited High current peak can saturate the LAN Magnetics, possibly damage it and other such as connector and patch panel
Testability	Simple and same as 802.3af	Complex Curve	Energy Limit Based PSE Added testing complexity and cost



Conclusion: Energy Limit Based For PoE+ System

- Energy Limit Based PSE Does Not Limit Peak Current During Input Transient → Possible LAN Magnetics Core Saturation and Data Corruption?
- Energy Limit Based PSE Does Not Limit Peak Current During Output Short Circuit → Possible Damage to Connector, Patch Panel, LAN Magnetics?
- Energy Limit Based PSE Creates Challenges For Compliant Testing



Conclusion: Current Limit Based For PoE+ System

- Current Limit Based PSE Can Easily Handle Simultaneous Input Voltage Transient and PD's Load Step
- Current Limit Based Assures PSE Port Current $\leq 926\text{mA}$ Maximum for $\leq 75\text{ms}$ During Input Transient
- Current Limit Based PSE Assures Port Current $\leq 926\text{mA}$ Maximum for $\leq 75\text{ms}$ During Output Short Circuit
- Current Limit Based PSE Eases Compliant Testing
- → Current Limit Based is the Recommended Technique to Limit the PSE Port Current in PoE+ System

